

# Chapter 2










## ***Digital Design and Computer Architecture, 2<sup>nd</sup> Edition***

David Money Harris and Sarah L. Harris

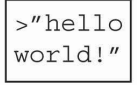

# Chapter 2 :: Topics

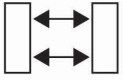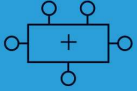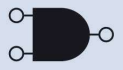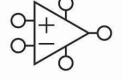
- Introduction
- Boolean Equations
- Boolean Algebra
- From Logic to Gates
- Multilevel Combinational Logic
- X's and Z's, Oh My
- Karnaugh Maps
- Combinational Building Blocks
- Timing

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	
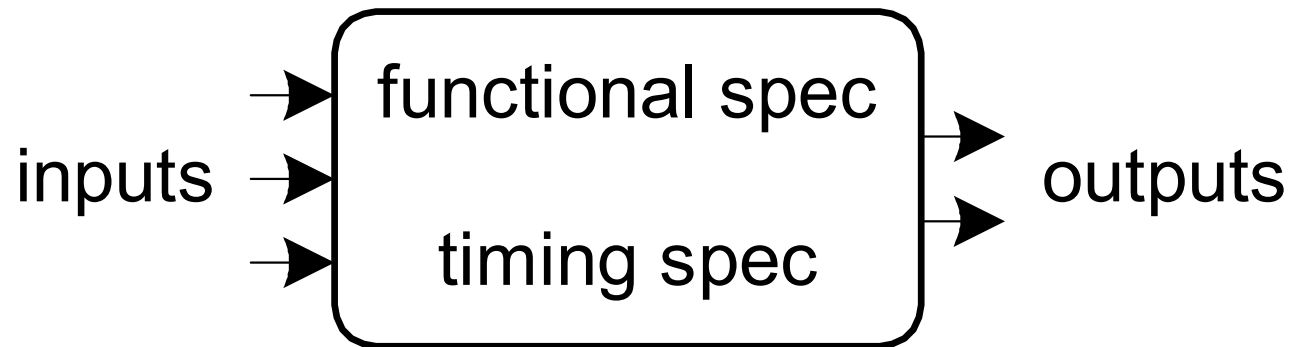
# Introduction


A logic circuit is composed of:

- Inputs
- Outputs
- Functional specification
- Timing specification



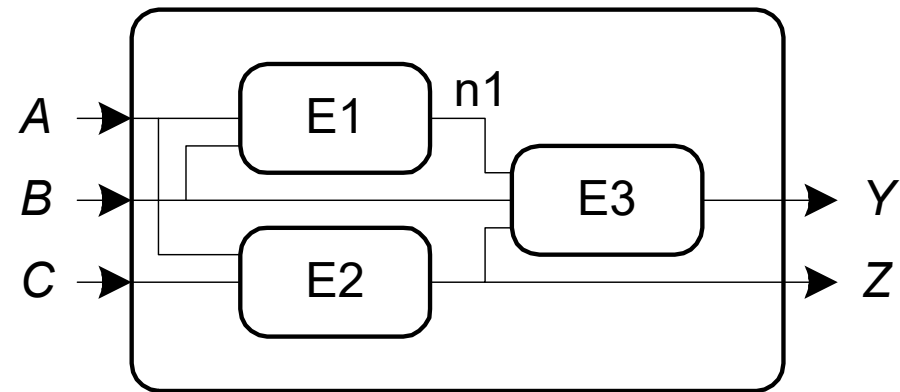
# Circuits

- Nodes
  - Inputs:  $A, B, C$
  - Outputs:  $Y, Z$
  - Internal:  $n1$
- Circuit elements
  - $E1, E2, E3$
  - Each a circuit



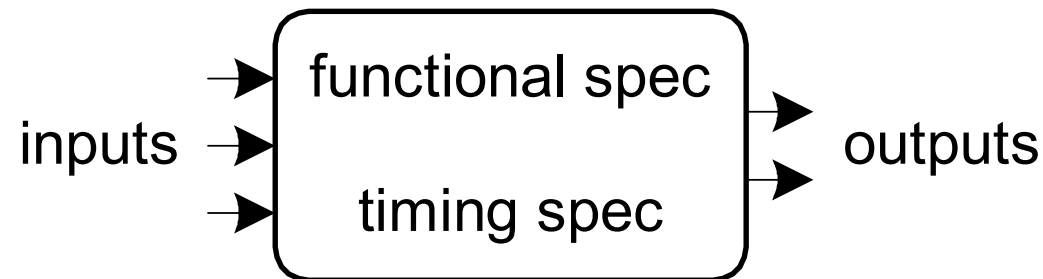
# Types of Logic Circuits

- **Combinational Logic**
  - Memoryless
  - Outputs determined by current values of inputs
- **Sequential Logic**
  - Has memory
  - Outputs determined by previous and current values of inputs



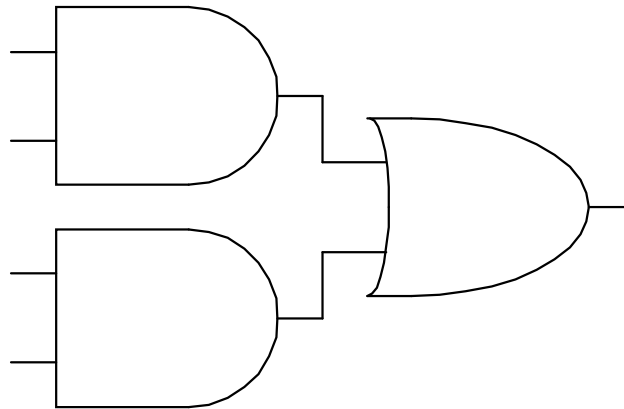
# Rules of Combinational Composition

- Every element is combinational
- Every node is either an input or connects to *exactly one* output
- The circuit contains no cyclic paths
- **Example:**


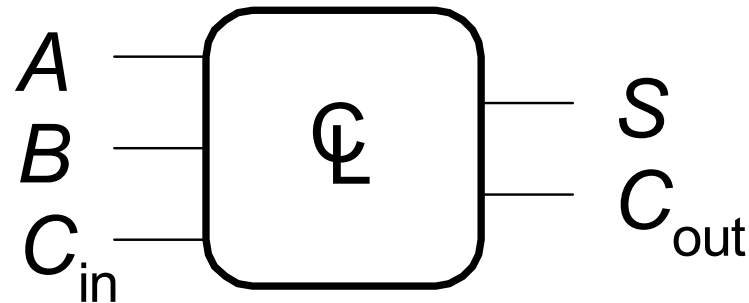
# Boolean Equations

- Functional specification of outputs in terms of inputs
- Example:**  $S = F(A, B, C_{in})$   
 $C_{out} = F(A, B, C_{in})$



$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

# Some Definitions

- Complement: variable with a bar over it  
 $\bar{A}, \bar{B}, \bar{C}$
- Literal: variable or its complement  
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- Implicant: product of literals  
 $AB\bar{C}, \bar{A}C, BC$
- Minterm: product that includes all input variables  
 $AB\bar{C}, A\bar{B}\bar{C}, ABC$
- Maxterm: sum that includes all input variables  
 $(A+B+C), (\bar{A}+B+\bar{C}), (\bar{A}+\bar{B}+C)$





# Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

<b>A</b>	<b>B</b>	<b>Y</b>	<b>minterm</b>	<b>minterm name</b>
0	0	0	$\overline{A} \overline{B}$	$m_0$
0	1	1	$\overline{A} B$	$m_1$
1	0	0	$A \overline{B}$	$m_2$
1	1	1	$A B$	$m_3$

$$Y = F(A, B) =$$

# Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

<b>A</b>	<b>B</b>	<b>Y</b>	<b>minterm</b>	<b>minterm name</b>
0	0	0	$\overline{A} \overline{B}$	$m_0$
0	1	1	$\overline{A} B$	$m_1$
1	0	0	$A \overline{B}$	$m_2$
1	1	1	$A B$	$m_3$

$$Y = F(A, B) =$$

# Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

<b>A</b>	<b>B</b>	<b>Y</b>	<b>minterm</b>	<b>minterm name</b>
0	0	0	$\overline{A} \overline{B}$	$m_0$
0	1	1	$\overline{A} B$	$m_1$
1	0	0	$A \overline{B}$	$m_2$
1	1	1	$A B$	$m_3$

$$Y = F(A, B) = \overline{A}B + AB = \Sigma(1, 3)$$

# Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a **maxterm**
- A maxterm is a sum (OR) of literals
- Each maxterm is FALSE for that row (and only that row)
- Form function by ANDing the maxterms for which the output is FALSE
- Thus, a product (AND) of sums (OR terms)

<b>A</b>	<b>B</b>	<b>Y</b>	<b>maxterm</b>	<b>maxterm name</b>
0	0	0	$A + B$	$M_0$
0	1	1	$A + \overline{B}$	$M_1$
1	0	0	$\overline{A} + B$	$M_2$
1	1	1	$\overline{A} + \overline{B}$	$M_3$

$$Y = F(A, B) = (A + B)(A + \overline{B}) = \Pi(0, 2)$$

# Boolean Equations Example

- You are going to the cafeteria for lunch
  - You won't eat lunch ( $E$ )
  - If it's not open ( $O$ ) or
  - If they only serve corndogs ( $C$ )
- Write a truth table for determining if you will eat lunch ( $E$ ).

$O$	$C$	$E$
0	0	
0	1	
1	0	
1	1	

# Boolean Equations Example

- You are going to the cafeteria for lunch
  - You won't eat lunch (E)
  - If it's not open (O) or
  - If they only serve corndogs (C)
- Write a truth table for determining if you will eat lunch (E).

O	C	E
0	0	0
0	1	0
1	0	1
1	1	0

# SOP & POS Form

- SOP – sum-of-products

O	C	E	minterm
0	0		$\overline{O} \overline{C}$
0	1		$\overline{O} C$
1	0		$O \overline{C}$
1	1		$O C$

- POS – product-of-sums

O	C	Y	maxterm
0	0		$O + C$
0	1		$O + \overline{C}$
1	0		$\overline{O} + C$
1	1		$\overline{O} + \overline{C}$

# SOP & POS Form

- SOP – sum-of-products

$O$	$C$	$E$	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

$$Y = OC$$

$$= \Sigma(2)$$

- POS – product-of-sums

$O$	$C$	$E$	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

$$Y = (O + C)(O + \overline{C})(\overline{O} + \overline{C})$$

$$= \Pi(0, 1, 3)$$





# Boolean Algebra

- Axioms and theorems to **simplify** Boolean equations
- Like regular algebra, but simpler: variables have only two values (1 or 0)
- **Duality** in axioms and theorems:
  - ANDs and ORs, 0's and 1's interchanged

# Boolean Axioms

Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

Theorem		Dual		Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements





# T1: Identity Theorem

- $B \cdot 1 = B$
- $B + 0 = B$

# T1: Identity Theorem

- $B \cdot 1 = B$
- $B + 0 = B$

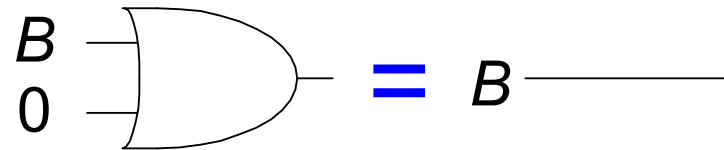
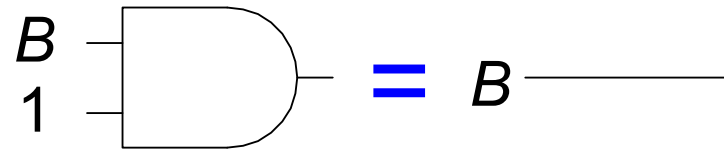


## T2: Null Element Theorem

- $B \cdot 0 = 0$
- $B + 1 = 1$

## T2: Null Element Theorem

- $B \cdot 0 = 0$
- $B + 1 = 1$

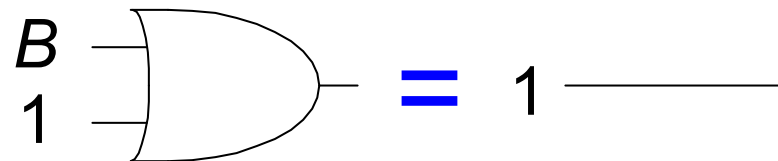
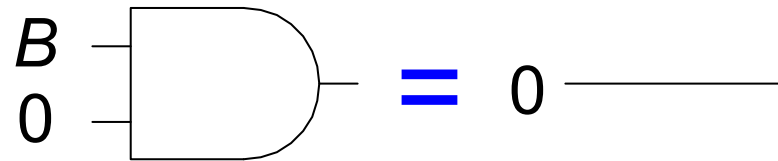


## T3: Idempotency Theorem

- $B \cdot B = B$
- $B + B = B$

## T3: Idempotency Theorem

- $B \cdot B = B$
- $B + B = B$

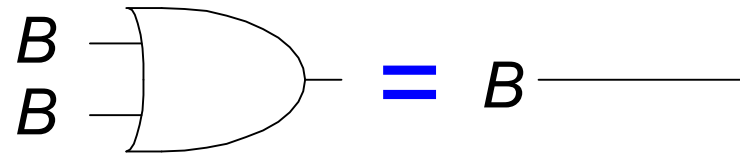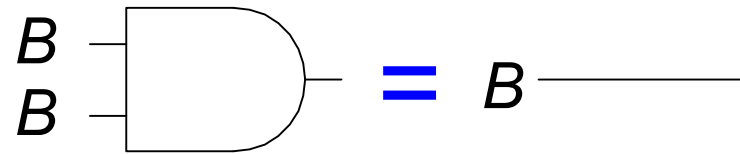




## T4: Identity Theorem

- $\overline{\overline{B}} = B$

## T4: Identity Theorem

- $\overline{\overline{B}} = B$


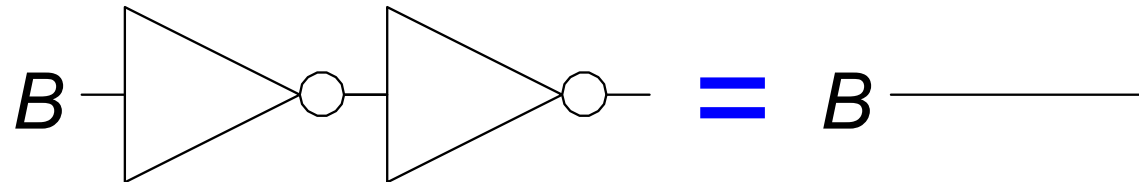


## T5: Complement Theorem

- $B \cdot \bar{B} = 0$
- $B + \bar{B} = 1$
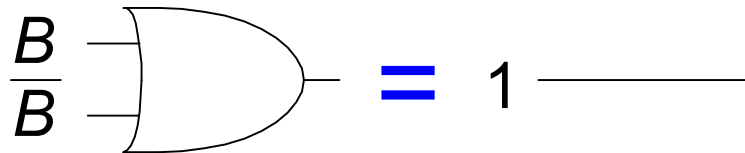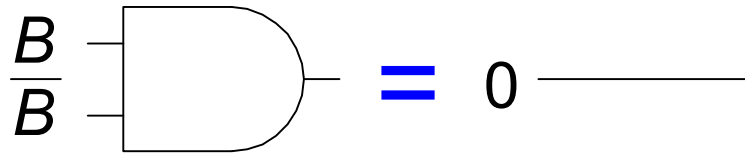
# T5: Complement Theorem

- $B \cdot \bar{B} = 0$
- $B + \bar{B} = 1$



# Boolean Theorems Summary

	Theorem		Dual	Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

# Boolean Theorems of Several Vars

Theorem		Dual		Name
T6	$B \bullet C = C \bullet B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \bullet C) + B \bullet D = B \bullet (C + D)$	T8'	$(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	T9'	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	T10'	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D)$ $= B \bullet C + \overline{B} \bullet D$	T11'	$(B + C) \bullet (\overline{B} + D) \bullet (C + D)$ $= (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots}$ $= (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots}$ $= (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2})$	De Morgan's Theorem

# Simplifying Boolean Equations

## Example 1:

- $Y = AB + \overline{A}B$

# Simplifying Boolean Equations

## Example 1:

- $Y = AB + \overline{A}B$   
 $= B(A + \overline{A})$  T8  
 $= B(1)$  T5'  
 $= B$  T1



# Simplifying Boolean Equations

## Example 2:

- $Y = A(AB + ABC)$



# Simplifying Boolean Equations

## Example 2:

- $$\begin{aligned} Y &= A(AB + ABC) \\ &= A(AB(1 + C)) && \text{T8} \\ &= A(AB(1)) && \text{T2'} \\ &= A(AB) && \text{T1} \\ &= (AA)B && \text{T7} \\ &= AB && \text{T3} \end{aligned}$$
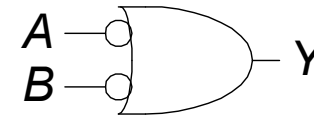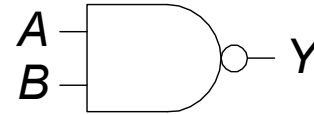
# DeMorgan's Theorem

- $Y = \overline{AB} = \overline{A} + \overline{B}$



- $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$

