

Logic Gates

- **Perform logic functions:**
 - inversion (NOT), AND, OR, NAND, NOR, etc.
- **Single-input:**
 - NOT gate, buffer
- **Two-input:**
 - AND, OR, XOR, NAND, NOR, XNOR
- **Multiple-input**


© Digital Design and Computer Architecture, 2nd Edition, 2012

Chapter 1 <53>



Single-Input Logic Gates


NOT

 

$$Y = \overline{A}$$

A	Y
0	1
1	0

BUF

 

$$Y = A$$

A	Y
0	0
1	1


© Digital Design and Computer Architecture, 2nd Edition, 2012

Chapter 1 <54>



Single-Input Logic Gates


NOT

 

$$Y = \overline{A}$$

A	Y
0	1
1	0

BUF

 


$$Y = A$$

A	Y
0	0
1	1



Two-Input Logic Gates


AND

 

$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR

 

$$Y = A + B$$


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1



FROM ZERO TO ONE

Two-Input Logic Gates


AND



$Y = AB$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


OR

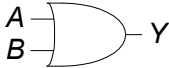

$Y = A + B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


© Digital Design and Computer Architecture, 2nd Edition, 2012 Chapter 1 <57>



FROM ZERO TO ONE

More Two-Input Logic Gates


XOR



$Y = A \oplus B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


NAND



$Y = \overline{AB}$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


NOR



$Y = \overline{A + B}$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


XNOR



$Y = \overline{A \oplus B}$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1


© Digital Design and Computer Architecture, 2nd Edition, 2012 Chapter 1 <58>



FROM ZERO TO ONE

More Two-Input Logic Gates


XOR

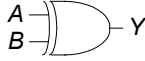

$Y = A \oplus B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


NAND



$Y = \overline{AB}$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


NOR

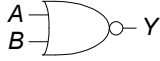

$Y = \overline{A + B}$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


XNOR

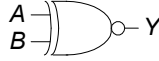

$Y = \overline{A \oplus B}$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1


© Digital Design and Computer Architecture, 2nd Edition, 2012 Chapter 1 <59>



FROM ZERO TO ONE

Multiple-Input Logic Gates


NOR3

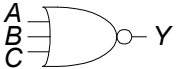

$Y = \overline{A+B+C}$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


AND4

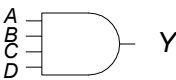

$Y = ABCD$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


© Digital Design and Computer Architecture, 2nd Edition, 2012 Chapter 1 <60>



FROM ZERO TO ONE

Multiple-Input Logic Gates


NOR3



$$Y = \overline{A+B+C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

AND4




$$Y = ABCD$$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

• Multi-input XOR: Odd parity

© Digital Design and Computer Architecture, 2nd Edition, 2012 Chapter 1 <61>




FROM ZERO TO ONE

Logic Levels

- Discrete voltages represent 1 and 0
- For example:
 - 0 = *ground* (GND) or 0 volts
 - 1 = V_{DD} or 5 volts
- What about 4.99 volts? Is that a 0 or a 1?
- What about 3.2 volts?

© Digital Design and Computer Architecture, 2nd Edition, 2012 Chapter 1 <62>




FROM ZERO TO ONE

Logic Levels

- *Range* of voltages for 1 and 0
- Different ranges for inputs and outputs to allow for *noise*


© Digital Design and Computer Architecture, 2nd Edition, 2012 Chapter 1 <63>



FROM ZERO TO ONE


What is Noise?

© Digital Design and Computer Architecture, 2nd Edition, 2012 Chapter 1 <64>



What is Noise?

- **Anything that degrades the signal**
 - E.g., resistance, power supply noise, coupling to neighboring wires, etc.
- **Example:** a gate (driver) outputs 5 V but, because of resistance in a long wire, receiver gets 4.5 V

 © Digital Design and Computer Architecture, 2nd Edition, 2012

Chapter 1 <65>





The Static Discipline



- With logically valid inputs, every circuit element must produce logically valid outputs
- Use limited ranges of voltages to represent discrete values

© Digital Design and Computer Architecture, 2nd Edition, 2012

Chapter 1 <66>



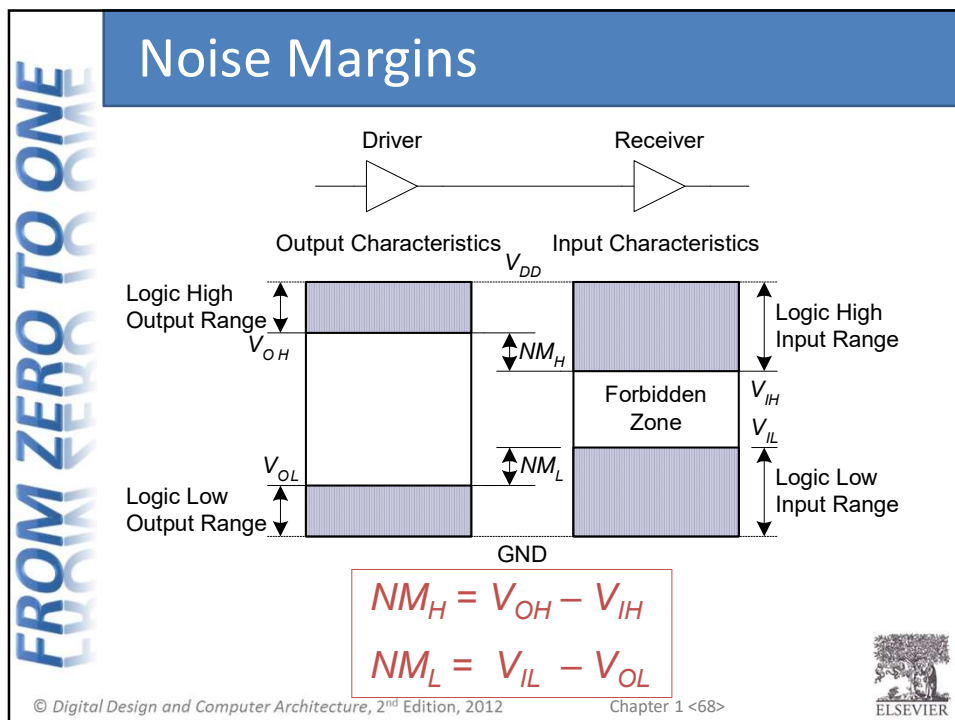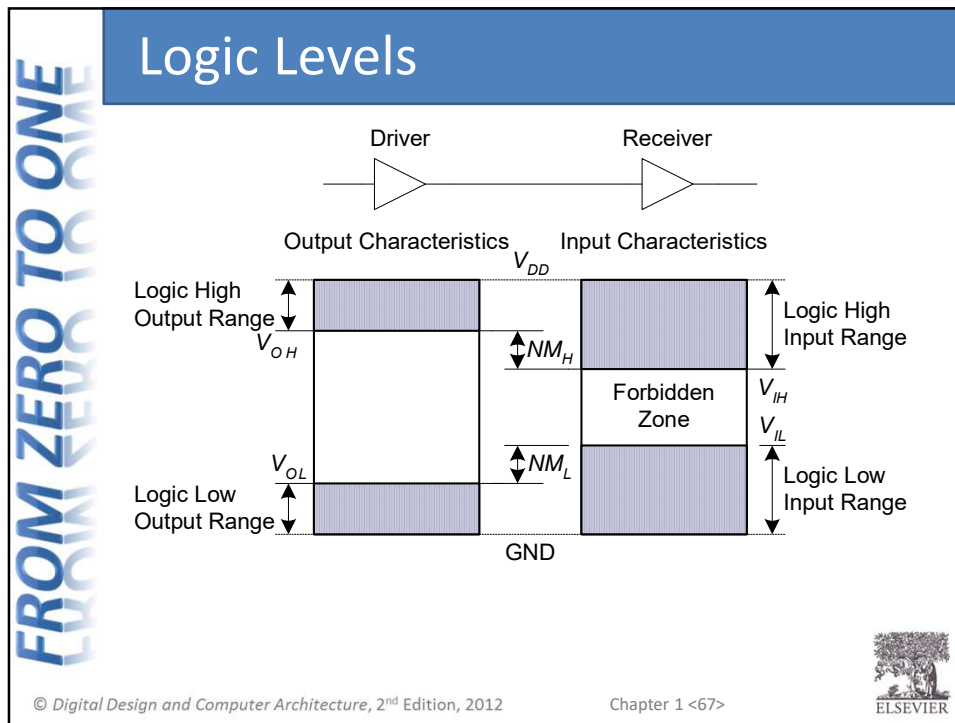

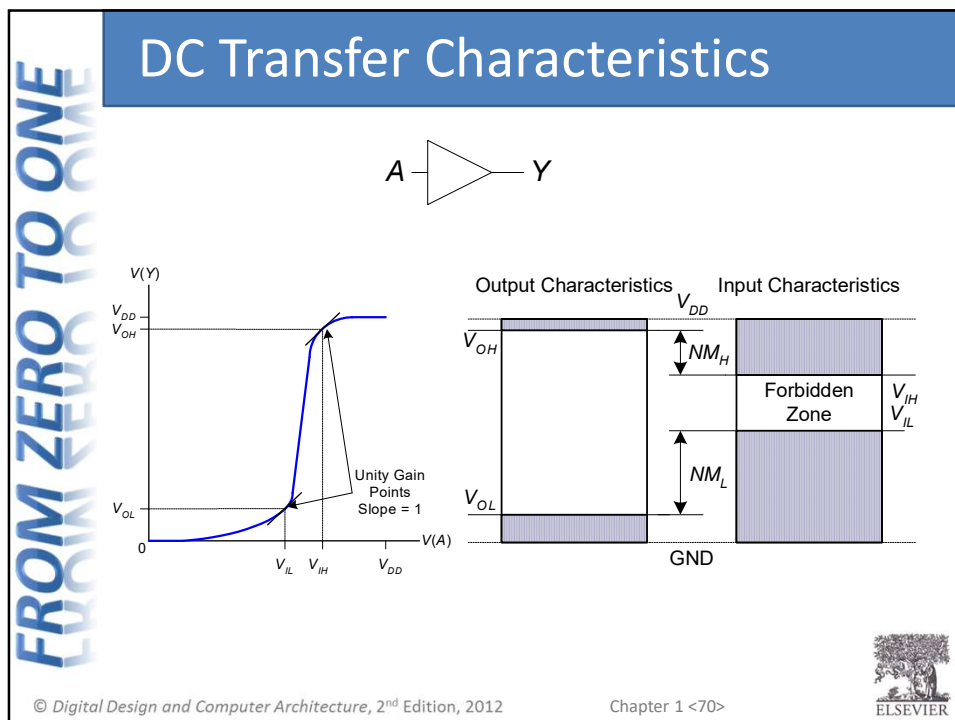 

FROM ZERO TO ONE



V_{DD} Scaling

- In 1970's and 1980's, V_{DD} = 5 V
- V_{DD} has dropped
 - Avoid frying tiny transistors
 - Save power
- 3.3 V, 2.5 V, 1.8 V, 1.5 V, 1.2 V, 1.0 V, ...
- Be careful connecting chips with different supply voltages

Chips operate because they contain magic smoke

Proof:

- if the magic smoke is let out, the chip stops working





© Digital Design and Computer Architecture, 2nd Edition, 2012 Chapter 1 <71>

FROM ZERO TO ONE

Logic Family Examples

Logic Family	V _{DD}	V _{IL}	V _{IH}	V _{OL}	V _{OH}
TTL	5 (4.75 - 5.25)	0.8	2.0	0.4	2.4
CMOS	5 (4.5 - 6)	1.35	3.15	0.33	3.84
LVTTL	3.3 (3 - 3.6)	0.8	2.0	0.4	2.4
LVC MOS	3.3 (3 - 3.6)	0.9	1.8	0.36	2.7



© Digital Design and Computer Architecture, 2nd Edition, 2012 Chapter 1 <72>